# **EESM 6000C System on chip laboratory**

# **Lab-3 FIR Report**

21106974 SHEN Zijun

#### Function specification

• 
$$y[t] = \Sigma (h[i] * x[t - i])$$

In signal processing, a finite-impulse-response, or finite impulse response models are generally linear dynamic models characterized by finite-order moving average representations, implying that their responses to impulse inputs go to zero after a finite number of time steps, equal to the model's memory length.


FIR filters can be discrete-time or continuous-time, and digital or analog.

$$egin{split} y[n] &= b_0 x[n] + b_1 x[n-1] + \dots + b_N x[n-N] \ &= \sum_{i=0}^N b_i \cdot x[n-i], \end{split}$$


#### Where:

- . x[n] is the input signal,
- . y[n] is the output signal,
- . N is the filter order; an Nth-order filter has N + 1 terms on the right-hand side
- .  $b_i$  is the value of the impulse response at the ith instant for  $0 \le I \le N$  of an Nth-order FIR filter. If the filter is a direct form FIR filter, then  $b_i$  is also a coefficient of the filter.

## Block Diagram

 

# Tap\_RAM / Data\_RAM

 

Tape RAM:

Tope address: 0x80 - 0xFF

EN = (AW[3]: \$] == 0) | (AR[3]: \$] == 0)& (AW[7] | AR[7])

Check if read/write address belongs to TapeRAM

WE = (AWvalid & & Wvalid == 1)? 4 b 1111: 4 b 0000; Check if address/data write is valid

A = AW[5=0] AW will >72, 4-bit left, still can represent the address of 11 tapes

Di = Wdata Data-in equals to wdata of AXI-Lite (hII) flow through TageRAM by avoilite)

Awready = 1 (PAM 尚有空間)

wready = 1 (Pata Buffer 前有 space)

# Data RAM:

EN = 55-tvalid (55-tlast = 0)


WE = (55-tready & 55\_idle)? 4'b 1111: 4'b 0000; (Ready to write New value & not finish)

A = (ap\_ctrl[2] && init\_addr < 6d44)? init\_addr: data\_A\_tmp;

If ap\_idle == 1, initialize the value in dataRAM.

Di = 55-tdata

 
FSM for ap\_ctrl: (ap.start, ap.done, ap\_idle)



- 1. The FSM in the top left is given to ap\_start, ap \_ stone, ap \_ dle, starting at INIT state, ap\_ctrl = {ap\_dle, ap\_stone, ap\_start} = 3'b100, when we Host end (testbench) program ap\_start, representing FIR, ap\_idle, down to IDLE state, ap\_ctrl = {ap\_idle, ap\_done, ap\_start} = 3'b000. When we finish the calculation of the last Y, send it to testbench alignment, and raise sm\_tlast, FIR completes the calculation and goes to DONE state, ap\_ctrl = {ap\_idle, ap\_done, ap\_start} = 3'b010. Since testbench needs to read the ap\_done signal, wait until read address == 0x00 reads to ap\_done before returning to the initial state.
- The FSM in the lower left corner specially produces the signal of ss\_iddle to take data \_ RAM as write enable, before the ss\_tlast, it will be 1, until the ss\_tlast, will enter the SS\_DONE state, ss\_idle = 0, means can not write again.
- 3. The FSM on the right is producing sm\_tlast. When the last Y is calculated, counter reaches data length, it goes to SM\_DONE state, and sm\_tlast raises a cycle.
 
### Operation explaining

The upper part of the picture is the y-wave graph that will appear before the operation pipeline. Each time ss\_tready is pulled high, representing stream-in new x [t] coming in the RAM. The next cycle can be found The sm\_tvalid, pulled high, represents that the calculated Y is taken to the testbench for comparison.




#### Resource usage


Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	190	0	0	53200	0.36
LUT as Logic	190	0	0	53200	0.36
LUT as Memory	0	0	0	17400	0.00
Slice Registers	224	0	0	106400	0.21
Register as Flip Flop	224	0	0	106400	0.21
Register as Latch	0	0	0	106400	0.00
F7 Muxes	0	0	0	26600	0.00
F8 Muxes	0	0	0	13300	0.00

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	140	0.00
RAMB36/FIFO*	0	0	0	140	0.00
RAMB18	0	0	0	280	0.00

#### Timing report




 

 


#### Simulation waveforms

#### Coefficient

 

#### X-in / Y-out

 

#### RAM access control

